



**NAVACHANA
UNIVERSITY**
a UGC recognized University

School: School of Engineering and Technology
Program/s: Computer science Engineering
Year: 1st **Semester:** 2nd
Examination: Mid-semester Examination
Examination year: May - 2023

Course Code: CS234

Course Name: Digital logic design

Date: 15/04/2023

Time: 2:00 pm to 4:00 pm

Total Marks: 40



Total Pages: 2

Instructions:

- Write each answer on a new page.
- Use of a calculator is permitted.
- *COs=Course Outcome mapping. # BTL=Bloom's Taxonomy Level mapping

| Que. 1 | <u>Attempt any FIVE</u> | Marks | COs* | BT* |
|--------|---|-------|------|--------------------------|
| a) | Design the circuit of half and full subtractor with a truth table, k-map and logic diagram. | 6 | CO3 | BT1 BT2 BT4 BT5 |
| b) | Design a 16:1 MUX using 4:1 MUX and explain the working. | 6 | CO3 | BT1 BT3 BT4 BT6 |
| c) | Design a 3 to 8 line decoder with truth table and logic diagram. How a decoder is different from MUX and DEMUX? | 6 | CO3 | BT2 BT3 BT5 BT6 |
| d) | Design a Binary to grey code converter with a truth table, K-map and logic circuit. | 6 | CO3 | BT1 BT2 BT4 BT5 |
| e) | Write a short note on the following: (i) Weighted and non-weighted code (ii) 2-bit magnitude comparator | 6 | CO2 | BT1 BT2 BT4 BT5 |
| f) | (i) Perform the following decimal subtraction in BCD by 9's complement. 305.5-168.8 (ii) Perform the addition in the XS-3 code: 247+359 | 6 | CO2 | BT1 BT3 BT4 BT6 |
| | | | | |

| | | | | |
|--------------|---|---|-------------|-------------------|
| Que.2 | Attempt any TWO | | | |
| a) | Define and explain the terms 'state table' and 'state diagram'. Compare and contrast Moore Model and Mealy Model. | 5 | CO2 | BT1 BT2 BT3 |
| b) | Draw the circuit diagram and discuss the state table for either SR flip flop or JK flip flop. | 5 | CO2, CO3 | BT3 BT4 |
| c) | Derive the state tables from following given state diagrams. | 5 | CO3 | BT4 BT5 BT6 |

  

*****End of Question Paper*****